

Binary Weighted DAC

Binary weighted digital-to-analogue converters are a type of data converter which converts a digital binary number into an equivalent analogue output signal proportional to the value of the digital number


The **Digital to Analogue Converter**, or **DAC**'s as they are more commonly known, are the opposite of the *Analogue to Digital Converter* we looked at in a previous tutorial. DAC's convert binary or non-binary numbers and codes into analogue ones with its output voltage (or current) being proportional to the value of its digital input number.

For example, we may have a 4-bit digital logic circuit that ranges from 0000 to 1111₂, (0 to F₁₆) which a DAC converts to a voltage output ranging from 0 to 10V.

Converting an “n”-bit digital input code into an equivalent analogue output voltage between 0 and some V_{MAX} value can be done in a number of ways, but the most common and easily understood conversion methods uses a weighted resistors and a summing amplifier, or a R-2R resistor ladder network and operational amplifier.

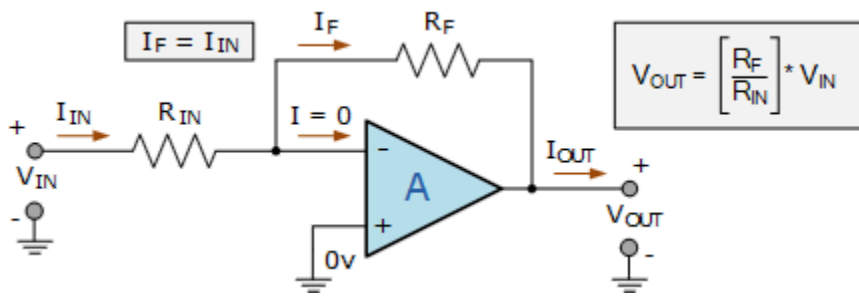Both *digital-to-analogue conversion* methods produce a weighted sum output, with the weights set by the resistive values used in the ladder networks contributing a different “weighted” amount to the signals output.





Then we can see that V_{OUT} is given as V_{IN} multiplied by the closed-loop Gain (A_{CL}), which is determined by the ratio of the feedback resistance, R_F to the input resistance, R_{IN} . So by altering the values of either R_F or R_{IN} we can change the closed-loop gain of the op-amp and therefore the value of V_{OUT} ($I_F \cdot R_F$) for a given input signal.

Here in this inverting operational amplifier example we have used a single input voltage signal, but what if we added another input resistor to combine two or more analogue signals into a single output, what would be the effect on the circuit and its gain.


Digital-to-Analogue Converter Summing Amplifier

By connecting multiple inputs to the negative terminal of the operational amplifier, we can convert the single input circuit from above into a *summing amplifier* or to be more precise, a “summing inverting voltage amplifier” circuit.

As the negative feedback created by the feedback resistor, R_F biases the inverting input of the op-amp at zero potential, any input signals are effectively electrically isolated from each other with the output being the inverted sum of all the input signals combined.

Thus a summing amplifier in the inverting mode produces the negative sum of any number of input voltages, whereas a non-inverting summing amplifier would produce the positive sum of any number of input voltages. Consider the circuit below.

Inverting Summing Amplifier Circuit

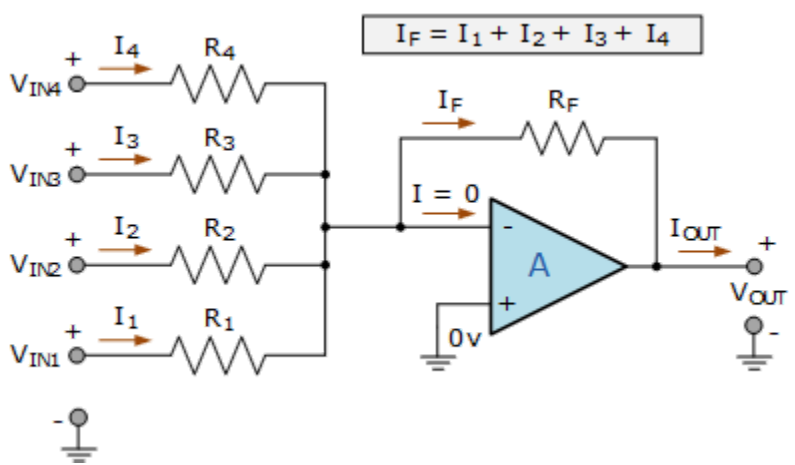

$$I_F = I_1 + I_2 + I_3 + I_4 = \frac{V_{IN1}}{R_1} + \frac{V_{IN2}}{R_2} + \frac{V_{IN3}}{R_3} + \frac{V_{IN4}}{R_4}$$

$$V_{OUT} = \frac{R_F}{I_F} \times V_{IN} = - \left(\frac{R_F}{R_1} V_{IN1} + \frac{R_F}{R_2} V_{IN2} + \frac{R_F}{R_3} V_{IN3} + \frac{R_F}{R_4} V_{IN4} \right)$$

$$\therefore V_{OUT} = - \frac{R_F}{R_{IN}} (V_{IN1} + V_{IN2} + V_{IN3} + V_{IN4})$$

Then we can see that the output voltage is an inverted, scaled sum of the four input voltages as each input voltage is multiplied by its corresponding gain and added to the next to produce the total output.


If all the resistances are the same and of an equal value, that is: $R_F = R_1 = R_2 = R_3 = R_4$, then each input channel will have a closed-loop voltage gain of unity (1) so the output voltage is given simply by:

$$V_{OUT} = -(V_{IN1} + V_{IN2} + V_{IN3} + V_{IN4})$$

So if we now assume that the four inputs of the summing amplifier are binary inputs with voltage values of either 0 or 5 volts (LOW or HIGH, 0 or 1) and we double the resistive values of each input resistor with regards to the previous one, we can produce an output condition which would be the weighted sum of these four input voltages creating the basic circuit for a 4-bit binary weighted digital-to-analogue converter, or 4-bit weighted D/A converter.

Labelling the four summing inputs as A, B, C, D and making $R_F = 1k\Omega$, with the four input resistors ranging from $1k\Omega$ to $8k\Omega$ (or multiples thereof), we can construct a simple 4-bit binary weighted analogue-to-digital converter circuit as shown.

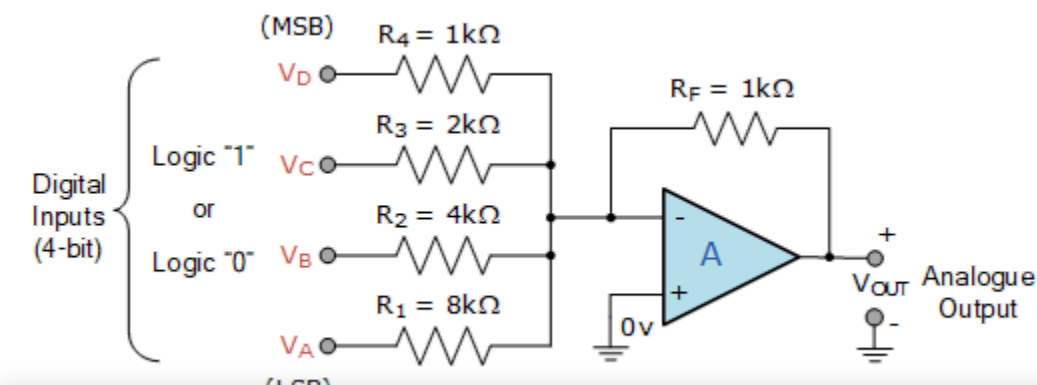4-bit Binary Weighted Digital-to-Analogue Converter



So if we set the “D” input resistance at 1kΩ, the “C” input resistance at 2kΩ (that is the double of D), the “B” input resistance at 4kΩ (double C), and the “A” input resistance at 8kΩ (double B), with the feedback resistance R_F set again at 1kΩ, then the transfer characteristic of the 4-bit binary weighted digital-to-analogue converter would be:

4-bit DAC Transfer Characteristic

$$V_{OUT} = - \left[\frac{R_F}{R_4} V_D + \frac{R_F}{R_3} V_C + \frac{R_F}{R_2} V_B + \frac{R_F}{R_1} V_A \right]$$
$$V_{OUT} = - \left[\frac{1k\Omega}{1k\Omega} V_D + \frac{1k\Omega}{2k\Omega} V_C + \frac{1k\Omega}{4k\Omega} V_B + \frac{1k\Omega}{8k\Omega} V_A \right]$$
$$V_{OUT} = - \left[1V_D + \frac{1}{2} V_C + \frac{1}{4} V_B + \frac{1}{8} V_A \right]$$

So we can see that if a TTL voltage of +5 volts (logic 1) is applied to the summing amplifiers input, V_D which represents the most significant bit (MSB), the op-amp’s gain will be R_F/R₄ = 1kΩ/1kΩ = 1 (unity). Thus with a 4-bit binary code of 1000 applied, the output of the digital-to-analogue converter circuit will be -5 volts.

Likewise, if +5 volts (logic 1) is applied to the summing amplifiers input V_C, the op-amp’s gain will be R_F/R₃ = 1kΩ/2kΩ = 1/2 (one half). So the 4-bit binary code of 0100 would produce an analogue output voltage of -2.5 volts.

Again with a logic “1” applied to the summing amplifiers input V_B, the op-amp’s gain will be R_F/R₂ = 1kΩ/4kΩ = 1/4 (one quarter) with the 4-bit binary code of 0010 producing an output voltage of -1.25 volts.

Finally a logic “1” applied to the summing amplifiers input, V_A which represents the least significant bit (LSB), the op-amp’s gain will therefore be R_F/R₁ = 1kΩ/8kΩ = 1/8 (one eighth) with the 4-bit binary code of 0001 producing an output voltage of -0.625 volts, (a 12.5% resolution).

The resolution of this simple 8-4-2-1 binary weighted digital-to-analogue converter will produce an output voltage change of 0.625 volts per 1-bit change in the binary number, and we can express this output voltage change in the following table.

4-bit Binary Weighted D/A Converter Output

Digital Inputs				V _{OUT} Expression	V _{OUT} in Volts
D	C	B	A	1*V _D + 1/2*V _C + 1/4*V _B + 1/8*V _A	
0	0	0	0	0*5 + 0*5 + 0*5 + 0*5	0
0	0	0	1	0*5 + 0*5 + 0*5 + 1/8*5	-0.625
0	0	1	0	0*5 + 0*5 + 1/4*5 + 0*5	-1.25



1	0	0	1	$1*5 + 0*5 + 0*5 + \frac{1}{8}*5$	-5.625
1	0	1	0	$1*5 + 0*5 + \frac{1}{4}*5 + 0*5$	-6.25
1	0	1	1	$1*5 + 0*5 + \frac{1}{4}*5 + \frac{1}{8}*5$	-6.875
1	1	0	0	$1*5 + \frac{1}{2}*5 + 0*5 + 0*5$	-7.50
1	1	0	1	$1*5 + \frac{1}{2}*5 + 0*5 + \frac{1}{8}*5$	-8.125
1	1	1	0	$1*5 + \frac{1}{2}*5 + \frac{1}{4}*5 + 0*5$	-8.75
1	1	1	1	$1*5 + \frac{1}{2}*5 + \frac{1}{4}*5 + \frac{1}{8}*5$	-9.375

Where the output voltages are all negative due to the inverting input of the summing amplifier.

By increasing the number of binary digits and the resistive summing network so that each resistor has a different weighting, the resolution of the analogue output voltage for a binary weighted digital-to-analogue converter can be increased.

For example, an 8-bit DAC with TTL +5 inputs would produce a resolution of 0.039 (1/128*V) volts, while a 12-bit DAC would be 0.00244 (1/2048*V) volts per step (1 LSB) change of the input binary (or non-binary) code.

Clearly then the disadvantage here is that a binary weighted resistor DAC requires a large range of high precision resistors (one per bit) for an “n”-bit DAC making it impractical (and expensive) for converters with more than a just a few bits of resolution.

But we can expand on this idea of a binary weighted digital-to-analogue circuit configuration which uses different value resistors one step further by converting it into a R-2R resistor ladder DAC which requires only two precision resistance values, namely R and 2R.

In the next turoial about **Digital-to-Analogue Converters**, we will look at how the *R-2R Digital-to-Analogue Converter* uses just two resistor values to convert a digital binary number into an analogue voltage output.

Read more Tutorials inCombinational Logic

- [1. Combinational Logic Circuits](#)
- [2. The Multiplexer](#)
- [3. The Demultiplexer](#)
- [4. Priority Encoder](#)
- [5. Binary Decoder](#)
- [6. Display Decoder](#)
- [7. Binary Adder](#)
- [8. Digital Comparator](#)
- [9. Binary Subtractor](#)
- [10. Bus Transceiver](#)
- [11. Transmission Gate](#)
- [12. Analogue to Digital Converter](#)
- [13. Binary Weighted DAC](#)
- [14. R-2R DAC](#)

4 Comments



Write your comment here

☐ Notify me of follow-up comments by email.

Submit

- Einar Örn Ásgersson

Is there a formula to find Rf if I know Vout?
I need to find out how big Rf has to be to get – 5 volts(Vout) when the digital inputs are 1 1 1 1

Posted on [August 24th 2022 | 11:32 am](#)
[Reply](#)

- Wayne Storr

Clearly, Vout = -9.375V when the digital inputs are 1 1 1 1 as Rf is normalised to 1kΩ. For Vout = -5 volts for the same input combination, then $R_f = 5/9.375 \times 1000 = 533 \text{ Ohms}$

Posted on [August 24th 2022 | 4:45 pm](#)
[Reply](#)

- Stephen Oswald

Can i use this circuit to design a 3 bit input binary weighted resistor DAC for reversing the operation of a 3 bit analogue to digital converter in the previous tutorial

Posted on [June 30th 2022 | 2:01 pm](#)
[Reply](#)

- M.CHANDRAMOHAN

I AM INTERESTED IN IT.

Posted on [June 19th 2022 | 8:19 am](#)
[Reply](#)

[Close](#)

